

LADDER ANALYSIS PROGRAM

FOR THE HP-41C



Varian EIMAC

**301 Industrial Way
San Carlos, California**

"BLAP": BACKWARDS LADDER ANALYSIS PROGRAM
BY GARY D. FREY W6XJ (3948)

ONE OF THE SIMPLEST WAYS TO ANALYZE A LADDER CIRCUIT IS TO ASSUME AN OUTPUT CURRENT; THEN WORK BACKWARDS THROUGH THE NETWORK OBTAINING ALL VOLTAGES AND CURRENTS IN TERMS OF THE ASSUMED OUTPUT CURRENT. FOR A LINEAR NETWORK, GAIN AND IMPEDANCE THROUGHOUT THE CIRCUIT ARE INDEPENDENT OF ACTUAL CURRENT AND VOLTAGE LEVELS AND THE RESPONSE (ALL VOLTAGES AND CURRENTS) DUE TO ONE VALUE OF EXCITATION MAY BE LINEARLY SCALED TO ANOTHER VALUE OF EXCITATION - FOR EXAMPLE YOU MIGHT WANT TO KNOW ALL VOLTAGES AND CURRENTS WITHIN A CIRCUIT FOR A SPECIFIC INPUT POWER IN ORDER TO DETERMINE THE VOLTAGE AND CURRENT RATINGS OF ALL THE COMPONENTS.

"BLAP" IS A COLLECTION OF SUBROUTINES FOR THE HP-41C WHICH EMPLOYS THE "BACKWARDS" ALGORITHM. THE LOAD CURRENT IS ASSUMED $1.0 + j0$ AMPERES FOR CONVENIENCE. THIS MAKES THE LOAD VOLTAGE R_L VOLTS FOR RESISTIVE LOAD R_L AND THE LOAD POWER IS R_L WATTS. WORKING BACK TOWARD THE GENERATOR; IF A SERIES IMPEDANCE IS ENCOUNTERED THE CURRENT IS UNCHANGED BUT THE VOLTAGE IS INCREASED BY THE DROP ACROSS THE SERIES IMPEDANCE ($V = V + I * Z_S$). IF A PARALLEL ADMITTANCE IS ENCOUNTERED THE VOLTAGE IS UNCHANGED BUT THE CURRENT IS INCREASED BY THE CURRENT FLOWING THROUGH THE SHUNT ADMITTANCE ($I = I + Y_P * V$). A LIBRARY OF 28 SERIES/PARALLEL TYPE ELEMENTS IS AVAILABLE (ALL SIMPLE SERIES/PARALLEL RLC COMBINATIONS, OPEN AND SHORTED TRANSMISSION LINE STUBS, AND SERIES AND SHUNT IMPEDANCES). TWO-PORT ELEMENTS MAY ALSO BE INCLUDED IN A LADDER CIRCUIT. FOUR TWO-PORT ELEMENTS ARE PROVIDED:

- GB RESISTIVE FEEDBACK GAIN BLOCK
- BG "BACKWARDS" GAIN BLOCK
- TL TRANSMISSION LINE
- TF IDEAL TRANSFORMER.

THE GAIN BLOCK IS A REASONABLE APPROXIMATION OF A SINGLE TRANSISTOR BROADBAND RESISTIVE FEEDBACK AMPLIFIER WHICH IS COMMONLY EMPLOYED IN MODERN CIRCUIT DESIGN (AVANTEK, OPTIMAX, W-J, ANZAC, ETC. AMPLIFIERS) AND INCLUDES THE COUPLING FROM LOAD TO SOURCE DUE TO THE INTENTIONAL FEEDBACK. BG IS THE SAME GAIN BLOCK IN THE REVERSE DIRECTION WHICH ALLOWS ANALYSIS IN EITHER DIRECTION OF ANY LADDER CIRCUIT, EVEN ONE INCLUDING AMPLIFIERS.

ALL ELEMENT SUBROUTINES ARE GIVEN GLOBAL LABELS SO THAT THEY MAY BE CALLED BY A SEPARATE PROGRAM WHICH DESCRIBES THE CIRCUIT. OTHER ELEMENT SUBROUTINES MAY BE ADDED TO "BLAP" -OR UNUSED ONES MAY BE DELETED. THE SUBROUTINE MUST COMPUTE THE INPUT CURRENT AND VOLTAGE IN TERMS OF THE "KNOWN" OUTPUT CURRENT AND VOLTAGE FOR THE ELEMENT BEING MODELED. A BRIEF STUDY OF THE REGISTER USAGE, THE APPENDIX, AND THE PROGRAM LISTING OF SOME OF THE SUBROUTINES USED SHOULD ENABLE THE USER TO GENERATE HIS OWN NEW ELEMENTS.

SIX "CDMPUTE AND PRINT" COMMANDS ARE
AVAILABLE IN THE BLAP PROGRAM:

- "RL" INITIALIZES LOAD AND "AVIEWS" FREQUENCY
- "RG" CDMPLTES AND "AVIEWS" GAIN
- "S" CDMPLTES AND "AVIEWS" FORWARD AND INPUT
"S" PARAMETERS (SF AND SI) IN DB
- "Z" CDMPLTES AND "AVIEWS" $Z=V/I$ AT ANY POINT
- "VP" "AVIEWS" V AT ANY POINT
- "IS" "AVIEWS" I AT ANY POINT

EXCEPT FOR "RL" WHICH INITIALIZES THE CIRCUIT (AND IS THE FIRST COMMAND USUALLY EXECUTED), THE V,I DATA IS NOT DISTURBED BY ANY OF THE COMMANDS SO THESE MAY BE EXECUTED ANYWHERE WITHIN THE CIRCUIT. "RG" OR "S" WILL NORMALLY BE THE LAST COMMAND EXECUTED. IN ADDITION TO THE SIX COMMANDS ABOVE, REGISTER USAGE IN BLAP IS COMPATIBLE WITH "PRPLOT" IN THE PRINTER ROM MAKING IT EASY TO PLOT ANY DESIRED CIRCUIT RESPONSE. "PRPLOT" SUPPLIES THE FREQUENCY TO THE CIRCUIT DESCRIPTION PROGRAM WHICH IN TURN RETURNS THE COMPUTED PARAMETER TO "PRPLOT".

USING BLAP

"BLAP" COMMANDS MAY BE MANUALLY EXECUTED TO ANALYZE A GIVEN CIRCUIT AT A SINGLE FREQUENCY; HOWEVER MOST OF THE TIME THE COMMANDS WILL BE STORED IN A PROGRAM IN ORDER TO "SWEEP" THE SELECTED RESPONSE VERSUS FREQUENCY. THE PRESENT ANALYSIS FREQUENCY -IN GHZ- MUST BE STORED IN REGISTER 08 SO THE CIRCUIT DESCRIPTION PROGRAM WILL USUALLY BE CONTAINED WITHIN A LOOP WHICH INCREMENTS R08 EITHER LINEARLY (ADDITIVE INCREMENTS) OR LOGARITHMICALLY (MULTIPLICATIVE INCREMENTS). "PRPLOT" AUTOMATICALLY PROVIDES A LINEARLY INCREMENTED FREQUENCY (X) LOOP. "PRPLOT" CAN BE MADE TO PROVIDE MULTIPLICATIVE INCREMENTS BY INITIALLY SPECIFYING A SMALL NON ZERO "X INCREMENT" THEN MULTIPLY R06 BY THE DESIRED INCREMENT IN THE CIRCUIT DESCRIPTION PROGRAM (R06 IS "PRPLOT" X). R17 CONTENTS ARE TACKED ONTO THE DISPLAY NAME FOR "Z", "VP", OR "IS" TO KEEP TRACK OF THE OUTPUT DATA. USUALLY START WITH 0 IN R17 AT LOAD END AND INCREMENT R17 BY ONE FOR EACH NEW ELEMENT ADDED. BEGIN THE PROGRAM WITH AN "RL" LOAD INITIALIZE COMMAND THEN WORK TOWARD THE GENERATOR USING THE ELEMENT COMMANDS TO DESCRIBE THE CIRCUIT - YOU MAY ASSIGN OFTEN-USED COMMANDS AND ELEMENTS TO USER KEYS TO SAVE TIME. OUTPUT COMMANDS MAY BE INSERTED ANYWHERE INTERMEDIATE RESULTS ARE DESIRED. THE LAST COMMAND WITHIN THE CIRCUIT DESCRIPTION LOOP WILL NORMALLY BE EITHER "RG" OR "S" TO OBTAIN THE OVERALL RESPONSE. EXAMPLES OF "BLAP" INCLUDING USING THE PLOTTER AND BOTH LINEAR AND LOG FREQUENCY SCALES ARE INCLUDED ALONG WITH THE PROGRAM LISTING TO AID THE USER IN CREATING HIS OWN CIRCUIT DESCRIPTION PROGRAMS.

COMPLEX NUMBER MATHEMATICS IS USUALLY REQUIRED FOR CIRCUIT ANALYSIS (EXCEPT AT DC OR FOR RESISTORS ONLY). "BLAP" CARRIES COMPLEX NUMBERS IN RECTANGULAR FORM FOR ALL OPERATIONS IN ORDER TO ACHIEVE A SPEED IMPROVEMENT OVER USING R-P AND P-R OPERATIONS. THE ROUTINES WITHIN "BLAP" EMPLOY ONLY STACK REGISTERS (X,Y,Z,T,L), R04, AND FLAG 14. "+" AND "-" EVEN SAVE "LAST X+JY" IN THE STACK (Z+JT). THE COMPLEX ARITHMETIC COMMANDS MAY BE EMPLOYED FOR GENERAL USE OUTSIDE OF "BLAP" - JUST REMEMBER THAT "1" USES REGISTER 04; ALL OTHER COMPLEX OPERATIONS AFFECT ONLY THE STACK.

QUICK REFERENCE GUIDE

>AT LEAST TWO MEMORY MODULES ARE REQUIRED<
BLAP COMMANDS:

NAME	DATA FORMAT	FUNCTION PERFORMED
RL	RL	INITIALIZE LOAD RESISTANCE
RG	RG	COMPUTE GAIN FOR RG GEN.
S	RG	COMPUTE SF AND SI FOR RL/RG
Z	(USE R17	COMPUTE IMPEDANCE
VP	AS INDEX	COMPUTE VOLTAGE TO GROUND
IS	MARKER)	COMPUTE SERIES CURRENT

BLAP ELEMENTS:

NAME	DATA FORMAT	FUNCTION PERFORMED
BG	R0 ↗ GDB	REVERSE GAIN BLOCK
GB	R0 ↗ GDB	TRANSISTOR GAIN BLOCK
TL	R0 ↗ θ 0 ↗ F0	TRANSMISSION LINE
TF	N1 ↗ N2	IDEAL TRANSFORMER
PRXS	R ↗ L ↗ C	PARALLEL RLC IN SERIES
PRXP	R ↗ L ↗ C	PARALLEL RLC IN PARALLEL
SRXP	R ↗ L ↗ C	SERIES RLC IN PARALLEL
SRXS	R ↗ L ↗ C	SERIES RLC IN SERIES
PLCS	L ↗ C	PARALLEL LC IN SERIES
PLCP	L ↗ C	PARALLEL LC IN PARALLEL
SLCP	L ↗ C	SERIES LC IN PARALLEL
SLCS	L ↗ C	SERIES LC IN SERIES
PRCS	R ↗ C	PARALLEL RC IN SERIES
PRCP	R ↗ C	PARALLEL RC IN PARALLEL
SRCF	R ↗ C	SERIES RC IN PARALLEL
SRCB	R ↗ C	SERIES RC IN SERIES
PRLS	R ↗ L	PARALLEL RL IN SERIES
PRLP	R ↗ L	PARALLEL RL IN PARALLEL
SRLP	R ↗ L	SERIES RL IN PARALLEL
SRLS	R ↗ L	SERIES RL IN SERIES
RP	R OHMS	R IN PARALLEL
RS	R	R IN SERIES
LP	L N _h	L IN PARALLEL
LS	L	L IN SERIES
CP	C PF	C IN PARALLEL
CS	C	C IN SERIES
ZP	R ↗ X	R+JX IN PARALLEL
ZS	R ↗ X	R+JX IN SERIES
OSTP	R0 ↗ θ 0 ↗ F0	OPEN STUB IN PARALLEL
OSTS	R0 ↗ θ 0 ↗ F0	OPEN STUB IN SERIES
SSTP	R0 ↗ θ 0 ↗ F0	SHORTED STUB IN PARALLEL
SSTS	R0 ↗ θ 0 ↗ F0	SHORTED STUB IN SERIES

COMPLEX MATH OPERATOR		OPERATION PERFORMED
	1	$X+JY=1/(X+JY)$
	/	$X+JY=(Z+JT)/(X+JY)$
	*	$X+JY=(X+JY)*(Z+JT)$
< "LAST X+JY" >	+	$X+JY=(X+JY)+(Z+JT)$
< SAVED IN Z+JT >	-	$X+JY=(Z+JT)-(X+JY)$

REGISTER USE:(MIN SIZE 020, DEG MODE, F00-04 CLEAR)

00	PLOTTER YMAX	10	PLOTTER XINC
01	PLOTTER YMIN	11	PLOT "NAME"
02	PLOT NNN.AAA	>12	RE(V)
03	PLOT CHARACTER	>13	IM(V)
<04	SCRATCH REGISTER	>14	RE(I)
05	PLOTTER "FIX" N	>15	IM(I)
06	PLOTTER FREQUENCY	>16	RL
07	PLOTTER "X UNITS"	>17	INDEX SYMBOL
<08	FREQUENCY GHZ	>18	SCRATCH REGISTER
09	PLOTTER XMAX	>19	SCRATCH REGISTER

GARY D. FREY W6XJ (3948)

001>LBL "BLAP"	061>LBL 01	121 SF 04
002 PFC 3948	062 RCL 15	122>LBL "SRXP"
003 PROMPT	063 RCL 04	123 SF 00
004>LBL "RL"	064 *	124>LBL "SRXS"
005 STO 16	065 ST+ 13	125>LBL 00
006 STO 12	066 RDN	126 SF01
007 1	067 RCL 14	127 GTO 00
008 STO 14	068 RCL 04	128>LBL "PLCS"
009 0	069 *	129 SF 04
010 STO 13	070 ST+ 12	130 GTO 00
011 STO 15	071 RDN	131>LBL "PLCP"
012 FIX 3	072 GTO 05	132 SF 04
013 "F="	073>LBL "TL"	133>LBL "SLCP"
014 ARCL 08	074 /	134 SF00
015 "H GrZ"	075 RCL 08	135>LBL "SLCS"
016 AVIEW	076 *	136>LBL 00
017 FIX 2	077 1	137 SF 03
018 RTN	078 F-R	138 SF 02
019>LBL "BG"	079 RDN	139 GTO 07
020 SF 00	080 STO 04	140>LBL "PRCS"
021>LBL "GB"	081 X<>Y	141 SF 04
022 20	082 ST/ 04	142 GTO 00
023 /	083 *	143>LBL "PRCP"
024 10 7 X	084 STO L	144 SF 04
025 2	085 R 7	145>LBL "SRCP"
026 /	086 RCL 13	146 SF 00
027 ENTER 7	087 RCL 12	147>LBL "SRCS"
028 X 7 2	088 RCL 15	148>LBL 00
029 LAST X	089 R 7	149 ENTER 7
030 ST+ X	090 ST* 12	150 SF 01
031 +	091 ST* 13	151 SF 03
032 1	092 ST* 15	152 GTO 07
033 +	093 X<> 14	153>LBL "PRLS"
034 SQRT	094 ST* 14	154 SF 04
035 +	095 X<> L	155 GTO 00
036 ST/ Z	096 ST* L	156>LBL "PRLP"
037 ST/ T	097 ST* Y	157 SF 04
038 *	098 RDN	158>LBL "SRLP"
039 STO 04	099 ST- 12	159 SF 00
040 FC?C 00	100 RDN	160>LBL "SRLS"
041 GTO 00	101 LAST X	161>LBL 00
042 RCL 13	102 ST+ 13	162 ENTER 7
043 RCL 12	103 RDN	163 SF 01
044 R 7	104 RCL 04	164 SF 02
045 ST/ Z	105 ST* Z	165 GTO 07
046 /	106 *	166>LBL "RP"
047 GTO 01	107 X<>Y	167 SF 00
048>LBL 00	108 CHS	168>LBL "RS"
049 -	109 GTO 05	169 ENTER 7
050 ST/ 12	110>LBL "TF"	170 ENTER 7
051 ST/ 13	111 /	171 SF 01
052 /	112 ST* 12	172 GTO 07
053 ST* 14	113 ST* 13	173>LBL "LP"
054 ST* 15	114 ST/ 14	174 SF 00
055 RCL 13	115 ST/ 15	175 LBL "LS"
056 RCL 12	116 RTN	176 ENTER 7
057 R 7	117>LBL "PRXS"	177 SF 02
058 ST* 12	118 SF 04	178 GTO 07
059 ST* 13	119 GTO 03	179>LBL "CP"
060 RDN	120>LBL "PRXP"	180 SF 00

181>LBL "CS"	241 *	301 RCL 19
182 SF 03	242 0	302 RCL 18
183>LBL 07	243>LBL 00	303 XEQ "L"
184 STO 04	244 FS?C 00	304 RDN
185 RDN	245 GTO 00	305 RDN
186 PI	246 FS?C 04	306 XEQ "/"
187 ST+ X	247 XEQ "1"	307 "SI"
188 RCL 03	248 RCL 15	308>LBL 00
189 *	249 RCL 14	309 "FDB"
190 *	250 XEQ "*"	310 R-P
191 LAST X	251 ST+ 12	311 LOG
192 -1 E3	252 RDN	312 20
193 /	253 ST+ 13	313 *
194 RCL 04	254 RTN	314 GTO 01
195 *	255>LBL 00	315>LBL "Z"
196 FC?C 03	256 FC?C 04	316 RCL 13
197 CLX	257 XEQ "1"	317 RCL 12
198 X#0?	258 RCL 13	318 RCL 15
199 1/X	259 RCL 12	319 RCL 14
200 XEQ 01	260 XEQ "*"	320 XEQ "/"
201 X<>Y	261>LBL 05	321 "Z"
202 FC?C 02	262 ST+ 14	322 GTO 00
203 CLX	263 RDN	323>LBL "VP"
204 XEQ 01	264 ST+ 15	324 RCL 13
205 +	265 RTN	325 RCL 12
206 X<>Y	266>LBL "S"	326 "V"
207 FC?C 01	267 SF 00	327 GTO 00
208 CLX	268>LBL "RG"	328>LBL "IS"
209 XEQ 01	269 STO 04	329 RCL 15
210 FS? 04	270 RCL 15	330 RCL 14
211 CHS	271 RCL 14	331 "I"
212 GTO 00	272 RCL 04	332>LBL 00
213>LBL 01	273 ST* Z	333 FIX 0
214 FC? 04	274 *	334 CF 29
215 RTN	275 RCL 13	335 ARCL 17
216 X#0?	276 RCL 12	336 FIX 2
217 1/X	277 XEQ "+"	337 SF 29
218 CHS	278 STO 18	338 R-P
219 RTN	279 X<>Y	339>LBL 01
220>LBL "ZF"	280 STO 19	340 RND
221 SF 00	281 X<>Y	341 X<>Y
222>LBL "ZS"	282 RCL 04	342 RND
223 X<>Y	283 RCL 16	343 X<>Y
224 GTO 00	284 *	344 "t="
225>LBL "OSTP"	285 SQRT	345 ARCL X
226 SF 00	286 ST+ X	346 "t<"
227>LBL "OSTS"	287 ST/ Z	347 ARCL Y
228 SF 04	288 /	348 AVIEW
229 GTO 01	289 XEQ "1"	349 RTN
230>LBL "SSTP"	290 "G"	350>LBL "/"
231 SF 00	291 FS? 00	351 SF 14
232>LBL "SSTS"	292 "SF"	352>LBL "1"
233>LBL 01	293 XEQ 00	353 STO 04
234 /	294 FC?C 00	354 X/ 2
235 RCL 03	295 RTN	355 RDN
236 *	296 RCL 13	356 CHS
237 TAN	297 RCL 12	357 X/ 2
238 X<>Y	298 2	358 ST+ T
239 FS? 04	299 ST* Z	359 X<>L
240 1/X	300 *	360 R/

361 ST/ 04
362 /
363 RCL 04
364 FCFC 14
365 RTN
366>LBL "x"
367 STD L
368 R↗
369 ST* L
370 R↗
371 ST* Z
372 R↗
373 ST* Z
374 ST* Y
375 X<>L
376 +
377 X<>T
378 RDN
379 -
380 RTN
381>LBL "+"
382 ST+ Z
383 RDN
384 ST+Z
385 RDN
386 RTN
387>LBL "--"
388 ST- Z
389 RDN
390 ST- Z
391 RDN
392 END 844 BYTES

APPENDIX

THE DERIVATION OF SOME OF THE "BLAP" ELEMENT SUBROUTINES IS PRESENTED IN THIS SECTION TO AID THE USER IN CREATING CUSTOMIZED SUBROUTINES FOR HIS NEEDS. FAMILIARITY WITH CIRCUIT ANALYSIS AND WITH USING THE HP-41C ARE THE ONLY PREREQUISITES.

SERIES-PARALLEL RLC'S

<pre> 0---R---L---C---0 +V1 +V2 -----> I1=I2 0-----0 "SRXS" I1=I2 V1=V2+I2*Z V1=V2+I2*(R+JWL-J/WC) </pre>	<pre> 0-----T-----0 +V1 R +V2 ---> L ---> I1 C I2 0-----0 "SRXP" V1=V2 I1=I2+V2*Y I1=I2+V2*1/Z </pre>
---	---

<pre> 0-----0 1 2 R L C 0---1---1---1---0 "PRXP" V1=V2 I1=I2+V2*Y I1=I2+V2*(1/R-J/WL+JWC) </pre>	<pre> 0---R---0 1 ---L--- 2 ---C--- 0-----0 "PRXS" I1=I2 V1=V2+I2*Z V1=V2+I2*1/Y </pre>
---	--


EITHER THE IMPEDANCE OF A SERIES RLC OR THE ADMITTANCE OF A PARALLEL RLC IS COMPUTED. "Z<>Y" TRANSFORMATION -IF NECESSARY- IS PERFORMED USING THE "1" COMMAND. FLAG 04 IS USED TO DISTINGUISH BETWEEN SERIES OR PARALLEL RLC CONNECTION WITHIN THE ELEMENT -F04 IS SET IF THE FIRST LETTER OF THE "NAME" IS "P" -. FLAG 00 IS USED TO DISTINGUISH BETWEEN SERIES OR PARALLEL USAGE OF THE ELEMENT WITHIN THE LADDER NETWORK -F00 IS SET IF THE LAST LETTER OF THE ELEMENT "NAME" IS "P" -. F01, F02, AND F03 ARE SET IF RESPECTIVELY R, L, OR C ARE PRESENT WITHIN THE BLOCK. THE FLAGS ARE TESTED LATER TO REMOVE ANY UNUSED ELEMENTS FROM THE GENERAL RLC ELEMENT. IF FLAGS 00 AND 04 MATCH, THE ELEMENT IS USED AS IS, OTHERWISE THE "1" COMMAND CONVERTS Z<>Y.

STUBS

TRANSMISSION LINE STUBS MAY ALSO SIMPLY BE REPRESENTED AS IMPEDANCES OR ADMITTANCES. THE SHORTED STUB IS REPRESENTED AS AN IMPEDANCE, WHILE THE OPEN STUB IS REPRESENTED AS AN ADMITTANCE.



 0-----0
1
"SSTS"
I1=I2
V1=V2+I2*Z
Z=0+JRC*TANO
O=00*F/F0



0-----0
1
"OSTP"
V1=V2
I1=I2+V2*Y
Y=0+J(1/RC)*TANO
O=00*F/F0

THE ONLY DIFFERENCE BETWEEN THE SHORTED STUB IMPEDANCE -Z- AND THE OPEN STUB ADMITTANCE -Y- IS R_0 VERSUS $1/R_0$. FLAG 04 IS SET FOR AN OPEN STUB -FIRST LETTER "O" AND FLAG 00 IS SET FOR PARALLEL STUB USAGE - LAST LETTER "P". ONCE THE STUB IMPEDANCE OR ADMITTANCE IS DETERMINED THE ELEMENT IS HANDLED WITHIN "BLAP" JUST LIKE A LUMPED IMPEDANCE OR ADMITTANCE.

ALMOST ANY PASSIVE FILTER MAY BE ANALYZED USING ONLY THE IMPEDANCE/ADMITTANCE ELEMENTS DESCRIBED ABOVE. "BLAP" DOES NOT PROVIDE ALL POSSIBLE RLC COMBINATIONS; HOWEVER, AND ALSO THE USER MIGHT FIND IT CONVENIENT AND FASTER TO CREATE COMBINATIONS OF EXISTING ELEMENTS. TWO EXAMPLES WHICH MIGHT WARRANT THEIR OWN COMMANDS ARE A QUARTZ CRYSTAL -SERIES RLC WITH A CAPACITOR IN PARALLEL- AND A REAL COIL OR RESISTOR -SERIES RL IN PARALLEL WITH A CAPACITOR. THESE ELEMENTS MAY BE REALIZED USING NORMAL "BLAP" COMMANDS ONLY IF THEY ARE USED AS PARALLEL ELEMENTS.

TWO-PORT ELEMENTS

ALL OF THE ELEMENTS DESCRIBED SO FAR HAVE EITHER IDENTICAL VOLTAGE ON EITHER SIDE -PARALLEL ELEMENT- OR IDENTICAL CURRENT ON EITHER SIDE -SERIES ELEMENT. MANY VERY USEFUL ELEMENTS MODIFY BOTH THE CURRENT AND VOLTAGE AND MUST BE CONSIDERED AS TWO-PORT NETWORKS -IN FACT THE ELEMENTS DESCRIBED ABOVE ARE SPECIAL TRIVIAL CASES OF TWO-PORT NETWORKS-. THE INPUT/OUTPUT RELATIONSHIP OF A TWO-PORT CAN BE DESCRIBED IN MANY EQUIVALENT WAYS - $Z, Y, G, H, S, ABCD$ - DEPENDING UPON THE CHOICE FROM I_1, V_1, I_2, V_2 OF THE PAIRS OF INDEPENDENT AND DEPENDENT VARIABLE PAIRS. IN "BLAP" I_2 , AND V_2 ARE THE INDEPENDENT VARIABLES SO WE ARE REALLY USING "BACKWARDS" $ABCD$ PARAMETERS. THE FOUR TWO-PORTS USED IN "BLAP" ARE PRESENTED BELOW:

```

0-----0
+V1 R0,G0,F0 +V2
I1-->      -->I2
0-----0

```

"TL"

```

I1=I2*COSG0+JV2*(1/R0)*SINO
V1=V2*COSG0+JI2*R0*SINO
G=00*F/F0

```

```

0-----0
+V1 N1:N2 +V2
I1-->      -->I2
0-----0


```

"TF"

```

I1=I2*N2/N1
V1=V2*N1/N2
N1, N2 +/-

```

 

"GB"

```

(RE*RF*I2+RE*V2)
V1= -----
RE-RF

```

```

(RE*I2+V2)
I1= -----
RE-RF

```



"EG"

```

V1=RF*I2+V2
I1=I2+V2/RE

```

```

R0=SQRT(RF*RE)
S21=(RE-RF)/(RE+R0)
G0B=20*LOG( S21 )

```

THE TWO-PORTS INCLUDED ARE ALL "IDEAL" ELEMENTS. THE TRANSMISSION LINE AND TRANSFORMER ARE LOSSLESS AND THE GAIN BLOCK IS BUILT USING AN IDEAL TRANSISTOR SUCH THAT THE AMPLIFIER PERFORMANCE IS SOLELY DETERMINED BY THE FEEDBACK RESISTORS. THE GAIN BLOCK HAS 180 DEGREES PHASE SHIFT AND IS A PERFECT MATCH IN A R0 OHM SYSTEM. "BLAP" ACTUALLY "DESIGNS" EACH GAIN BLOCK - COMPUTES RF AND RE FOR SPECIFIED DB GAIN AND SYSTEM RESISTANCE R0-. SIMULTANEOUS PERFECT MATCH WITH THE GAIN BLOCK IS ONLY POSSIBLE IF THE GENERATOR AND LOAD IMPEDANCES ARE EQUAL. THE "GB" MAY ALWAYS BE CASCADED WITH A TRANSFORMER OR MATCHING NETWORK TO OBTAIN ANY COMBINATION OF SOURCE AND LOAD IMPEDANCES. THE GAIN BLOCK IS UNCONDITIONALLY STABLE SINCE THE INPUT AND OUTPUT MATCH IS PERFECT IN A R0 OHM SYSTEM AND THE REVERSE ISOLATION IS GREATER THAN THE FORWARD GAIN.

CANDIDATES FOR OTHER TWO-PORT ELEMENTS ARE LIMITLESS. LOSSY TRANSMISSION LINE, NON-IDEAL TRANSFORMERS, AND GAIN BLOCKS HAVING "REAL" TRANSISTORS ARE OBVIOUS EXAMPLES. HAPPY PROGRAMMING!